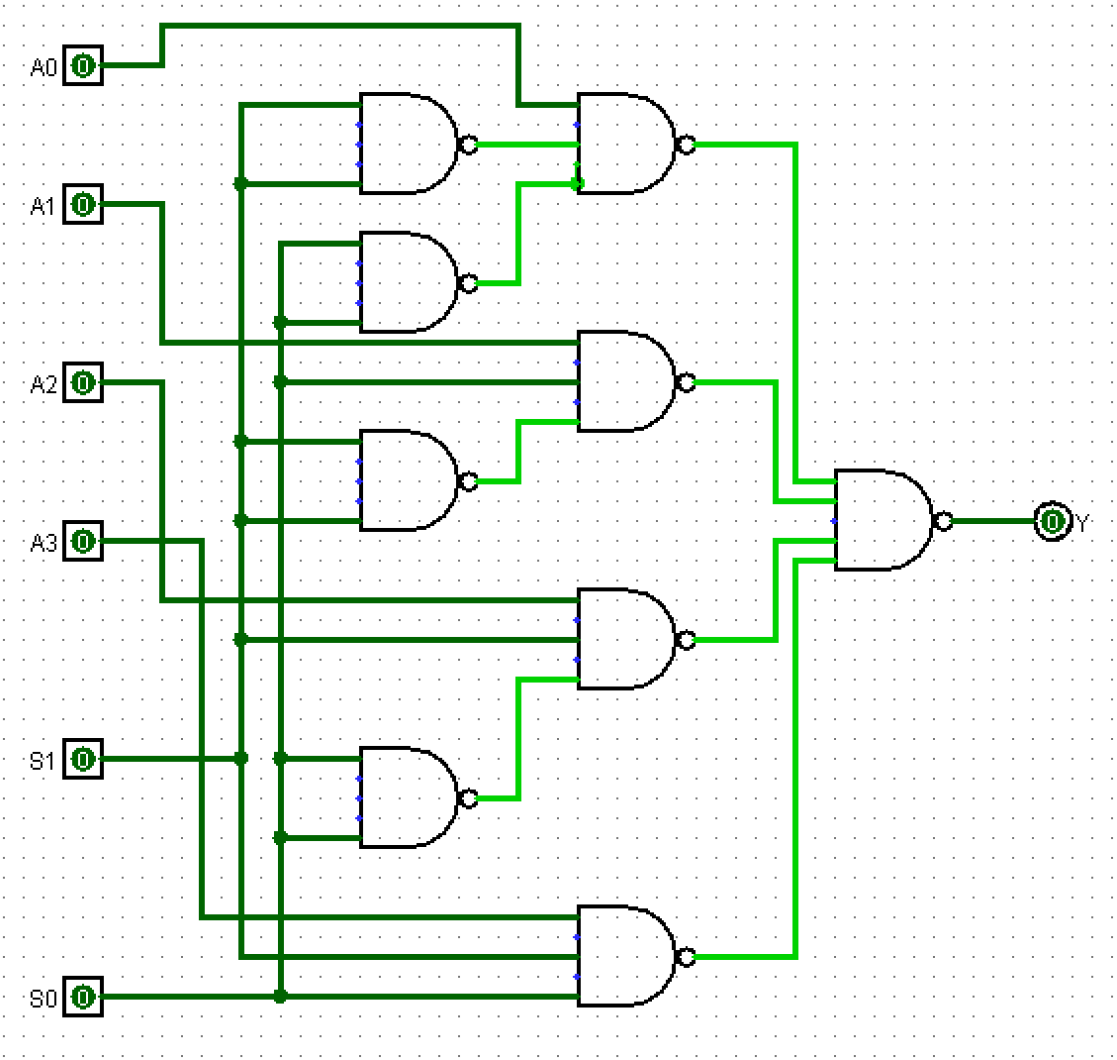


CT Unit 3: Logic Gates Project Group: Name: Grace Wang and Abigail Eng

Assignment #2

1. drawing the logic circuit diagram using *Logisim*,



S1	S0	A3	A2	A1	A0	Y
0	0	0	0	0	0	0
0	0	0	0	0	1	1
0	0	0	0	1	0	0
0	0	0	0	1	1	1
0	0	0	1	0	0	0
0	0	0	1	0	1	1
0	0	0	1	1	0	0
0	0	0	1	1	1	1
0	0	1	0	0	0	0

0	0	1	0	0	1	1
0	0	1	0	1	0	0
0	0	1	0	1	1	1
0	0	1	1	0	0	0
0	0	1	1	0	1	1
0	0	1	1	1	0	0
0	0	1	1	1	1	1
0	1	0	0	0	0	0
0	1	0	0	0	1	0
0	1	0	0	1	0	1
0	1	0	0	1	1	1
0	1	0	1	0	0	0
0	1	0	1	0	1	0
0	1	0	1	1	0	1
0	1	0	1	1	1	1
0	1	1	0	0	0	0
0	1	1	0	0	1	0
0	1	1	0	1	0	1
0	1	1	0	1	1	1
0	1	1	1	0	0	0
0	1	1	1	0	1	0
0	1	1	1	1	0	1
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	0	0	0	1	0
1	0	0	0	1	0	0
1	0	0	0	1	1	0
1	0	0	1	0	0	1
1	0	0	1	0	1	1
1	0	0	1	1	0	1
1	0	0	1	1	1	1
1	0	1	0	0	0	0
1	0	1	0	0	1	0
1	0	1	0	1	0	0
1	0	1	0	1	1	0
1	0	1	1	0	0	1
1	0	1	1	0	1	1
1	0	1	1	1	0	1

1	0	1	1	1	1	1
1	1	0	0	0	0	0
1	1	0	0	0	1	0
1	1	0	0	1	0	0
1	1	0	0	1	1	0
1	1	0	1	0	0	0
1	1	0	1	0	1	0
1	1	0	1	1	0	0
1	1	0	1	1	1	0
1	1	1	0	0	0	1
1	1	1	0	0	1	1
1	1	1	0	1	0	1
1	1	1	0	1	1	1
1	1	1	1	0	0	1
1	1	1	1	0	1	1
1	1	1	1	1	0	1
1	1	1	1	1	1	1

3. writing the Boolean function of each output variable, and

Output:

Format:

Too many inputs for table.

$d e f + c e \bar{f} + b \bar{e} f + a \bar{e} \bar{f}$

4. explaining the possible usage of the logic circuits.

By reading the input of S1-A0 and the output of Y, we notice that when $S = n$, $Y = A(n)$ and $n = 0 - 3$. So, the logic circuit is a 4-bit incrementing circuit.